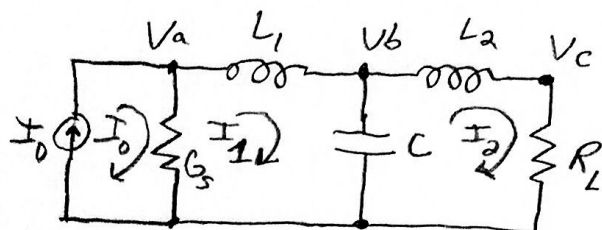


4.3b.



$$L_1 \frac{dI_1}{dt} + \frac{1}{C} \int (I_1 - I_2) dt + \frac{(I_1 - I_0)}{G_s} = 0$$


$$L_2 \frac{dI_2}{dt} + I_2 R_L + \frac{1}{C} \int (I_2 - I_1) dt = 0$$

Node V_a : $I_0 = V_a G_s + \frac{1}{L_1} \int (V_a - V_b) dt \rightarrow I_0 - V_a G_s - \frac{1}{L_1} \int (V_a - V_b) dt = 0$

Node V_b : $\frac{1}{L_1} \int (V_b - V_a) dt + C \frac{dV_b}{dt} + \frac{1}{L_2} \int (V_b - V_c) dt = 0$


Node V_c : $\frac{V_c}{R_L} + \frac{1}{L_2} \int (V_c - V_b) dt = 0$

4.3c.

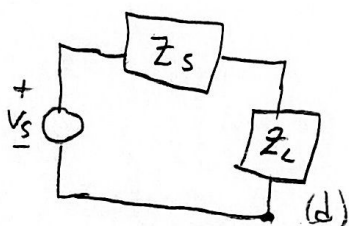

$$I_L = \frac{V_s}{Z_s + Z_L} \quad \text{Current through the load impedance}$$
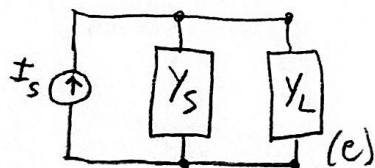
$$V_L = V_s \left(\frac{Z_L}{Z_s + Z_L} \right)$$



$$V_L = \frac{I_s}{Y_s + Y_L}$$

$$I_s = V_s Y_s, \quad Y_s = Z_s^{-1} \rightarrow I_s = \frac{V_s}{Z_s}$$

$$V_L = \frac{I_s}{Y_s + Y_L} \rightarrow \frac{(V_s/Z_s)}{(Z_s^{-1}) + (Z_L^{-1})} = V_s \left(\frac{Z_L}{Z_s + Z_L} \right)$$

Current through load admittance:

$$I_L = V_L Y_L = V_s \left(\frac{Z_L}{Z_s + Z_L} \right) (Z_L^{-1}) = \frac{V_s}{Z_s + Z_L}$$

I_L is the same for the current flowing through the load impedance and the current through the load admittance.

V_L is also the same for the voltage across the load impedance and the voltage across the load admittance.

4.3 d. For the current in the circuit:

$$I = \frac{V_s}{Z_s + Z_L} \quad \text{where } Z_s = R_s + jX_s \text{ and } Z_L = R_L + jX_L$$

$$I = \frac{V_s}{(R_s + jX_s) + (R_L + jX_L)} = \frac{V_s}{(R_s + R_L) + j(X_s + X_L)}$$

For power to the load, $W_L = \frac{R_L}{2} I I^*$

$$I^* = \left[\frac{V_s}{(R_s + R_L) + j(X_s + X_L)} \right]^* = \left[\frac{V_s}{(R_s + R_L) + j(X_s + X_L)} \right] \left[\frac{(R_s + R_L) - j(X_s + X_L)}{(R_s + R_L) - j(X_s + X_L)} \right]$$

$$I^* = \frac{V_s [(R_s + R_L) - j(X_s + X_L)]}{(R_s + R_L)^2 + (X_s + X_L)^2}$$

$$W_L = \frac{R_L}{2} \left[\frac{V_s}{(R_s + R_L) + j(X_s + X_L)} \right] \left[\frac{V_s [(R_s + R_L) - j(X_s + X_L)]}{(R_s + R_L)^2 + (X_s + X_L)^2} \right]$$

$$= \frac{R_L}{2} \left[\frac{V_s}{(R_s + R_L)^2 + (X_s + X_L)^2} \right]$$

For max power to load: $\frac{\partial W_L}{\partial X_L} = 0$ and $\frac{\partial W_L}{\partial R_L} = 0$

$$\frac{\partial W_L}{\partial X_L} = \frac{\partial}{\partial X_L} \left(\frac{R_L}{2} \left[\frac{V_s}{(R_s + R_L)^2 + (X_s + X_L)^2} \right] \right) = 0$$

$$= \frac{-R_L V_s (X_s + X_L)}{[(R_s + R_L)^2 + (X_s + X_L)^2]^2} \rightarrow -R_L V_s (X_s + X_L) = 0, \quad X_L = -X_s$$

$$\frac{\partial W_L}{\partial R_L} = \frac{\partial}{\partial R_L} \left(\frac{R_L}{2} \left[\frac{V_s}{(R_s + R_L)^2 + (X_s + X_L)^2} \right] \right) = 0$$

$$= \frac{V_s}{2} \left[\frac{-2R_L (R_s + R_L) + [(R_s + R_L)^2 + (X_s + X_L)^2]}{[(R_s + R_L)^2 + (X_s + X_L)^2]^2} \right] = 0$$

$$-2R_L(R_S + R_L) + [(R_S + R_L)^2 + (X_S + X_L)^2] = 0$$

$$R_S X_L = -X_S$$


$$-2R_L(R_S + R_L) + [(R_S + R_L)^2 + 0] = 0$$

$$-2R_L R_S - 2R_L^2 + R_S^2 + R_L^2 + 2R_L R_S = R_S^2 - R_L^2 = 0, \quad R_L = R_S$$

Max power to the load when $R_L = R_S$ and $X_L = -X_S$

$$Z_L = R_L + jX_L = R_S + j(-X_S) = R_S - jX_S = (R_S + jX_S)^* = Z_S^*$$

4.6 e.

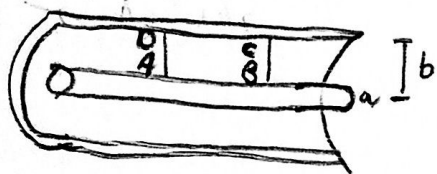

$$\oint_{ABCD} E \cdot dl = -j\omega \int_S B \cdot dS$$

$$\int_S B \cdot dS = I L_e dz$$

for $E_z = I (Z_{\text{inner}})_{\text{outer}}$

$$\oint_{ABCD} E \cdot dl = -j\omega I L_e dz$$

inner surface of the outer conductor

$$E_z = I \left(\frac{R_{sb}}{2\pi b} + \frac{j\omega L_{ib}}{2\pi b} \right)$$

b = radius of outer conductor

R_{sb} = resistance

L_{ib} = inductance

for $E_z = -I (Z_{\text{inner}})_{\text{inner}}$ outer surface of inner conductor

$$E_z = -I \left(\frac{R_{sa}}{2\pi a} + \frac{j\omega L_{ia}}{2\pi a} \right)$$

a = radius of inner conductor

R_{sa} = resistance

L_{ia} = inductance

$$\oint_{ABCD} E \cdot dl = -j\omega I L_e dz$$

$$I \left(\frac{R_{sa}}{2\pi a} + \frac{j\omega L_{ia}}{2\pi a} \right) dz + V_{CB} + I \left(\frac{R_{sb}}{2\pi b} + \frac{j\omega L_{ib}}{2\pi b} \right) dz - V_{DA} = -j\omega I L_e dz$$

$$V_{DA} - V_{CB} = I \left(j\omega L_e + \frac{R_{sa}}{2\pi a} + \frac{j\omega L_{ia}}{2\pi a} + \frac{R_{sb}}{2\pi b} + \frac{j\omega L_{ib}}{2\pi b} \right) dz$$

$$V_{DA} - V_{CB} = 0$$

For current from C to D,

$$I_C - I_D = j\omega(Cdz)V$$

$$C = \frac{2\pi\epsilon}{\ln(b/a)} \frac{f}{m}$$

$$I_C - I_D = j\omega \left(\frac{2\pi\epsilon dz}{\ln(b/a)} \right) V \quad \text{matches capacitance shown in Fig. P4.6e}$$