

11.1.1.

Voltage Law:

$$\begin{aligned}
 \text{Loop 1: } & \text{Re}[\tilde{V}_0 e^{j\omega t}] - L \frac{d}{dt} \text{Re}[\tilde{I}_1 e^{j\omega t}] - \frac{1}{C} \int (\text{Re}[\tilde{I}_1 e^{j\omega t}] - \text{Re}[\tilde{I}_2 e^{j\omega t}]) dt = 0 \\
 & = \text{Re}[\tilde{V}_0 e^{j\omega t}] - L (j\omega) \text{Re}[\tilde{I}_1 e^{j\omega t}] - \frac{1}{C} \int (\text{Re}[\tilde{I}_1 e^{j\omega t}] - \text{Re}[\tilde{I}_2 e^{j\omega t}]) dt = 0 \\
 & = \text{Re}[\tilde{V}_0 - j\omega L \tilde{I}_1 - \frac{1}{C} \int (\tilde{I}_1 - \tilde{I}_2) dt] e^{j\omega t} = 0 \\
 & = \text{Re}[\tilde{V}_0 - j\omega L \tilde{I}_1 - \tilde{V}_1] e^{j\omega t} = 0 \\
 & = \tilde{V}_0 - j\omega L \tilde{I}_1 - \tilde{V}_1 = 0 \rightarrow \tilde{V}_1 = \tilde{V}_0 - j\omega L \tilde{I}_1
 \end{aligned}$$

$$\begin{aligned}
 \text{Loop 2: } & -\frac{1}{C} \int (\text{Re}[\tilde{I}_2 e^{j\omega t}] - \text{Re}[\tilde{I}_1 e^{j\omega t}]) dt - L_2 \frac{d}{dt} \text{Re}[\tilde{I}_2 e^{j\omega t}] - Z_L \text{Re}[\tilde{I}_2 e^{j\omega t}] = 0 \\
 & = \frac{1}{C} \int (\text{Re}[\tilde{I}_2 e^{j\omega t}] - \text{Re}[\tilde{I}_1 e^{j\omega t}]) dt - L_2 (j\omega) \text{Re}[\tilde{I}_2 e^{j\omega t}] - Z_L \text{Re}[\tilde{I}_2 e^{j\omega t}] = 0 \\
 & = \text{Re}[\frac{1}{C} \int (\tilde{I}_2 - \tilde{I}_1) dt - L_2 (j\omega) \tilde{I}_2 - Z_L \tilde{I}_2] e^{j\omega t} = 0 \\
 & = \text{Re}[-(-\tilde{V}_1) - j\omega L_2 \tilde{I}_2 - Z_L \tilde{I}_2] e^{j\omega t} = 0 \\
 & \tilde{V}_1 - j\omega L_2 \tilde{I}_2 - \tilde{V}_2 = 0 \rightarrow \tilde{V}_2 = \tilde{V}_1 - j\omega L_2 \tilde{I}_2
 \end{aligned}$$

Should justify the -> step that led to this.

Current Law:

$$\begin{aligned}
 \text{Node 1: } & \frac{1}{Z_1} \int (\text{Re}[\tilde{V}_1 e^{j\omega t}] - \text{Re}[\tilde{V}_0 e^{j\omega t}]) dt + \frac{1}{Z_2} \int (\text{Re}[\tilde{V}_1 e^{j\omega t}] - \text{Re}[\tilde{V}_2 e^{j\omega t}]) dt \\
 & + C \frac{d}{dt} \text{Re}[\tilde{V}_1 e^{j\omega t}] = 0 \\
 & = \text{Re}[\frac{1}{Z_1} \int (\tilde{V}_1 - \tilde{V}_0) dt + \frac{1}{Z_2} \int (\tilde{V}_1 - \tilde{V}_2) dt + C (j\omega) \tilde{V}_1] e^{j\omega t} = 0 \\
 & = \text{Re}[-\tilde{I}_1 + \tilde{I}_2 + j\omega C \tilde{V}_1] e^{j\omega t} = 0 \\
 & = -\tilde{I}_1 + \tilde{I}_2 + j\omega C \tilde{V}_1 = 0 \rightarrow \tilde{I}_2 = \tilde{I}_1 - j\omega C \tilde{V}_1
 \end{aligned}$$

$$\begin{aligned}
 \text{Node 2: } & \frac{1}{Z_2} \int (\text{Re}[\tilde{V}_2 e^{j\omega t}] - \text{Re}[\tilde{V}_1 e^{j\omega t}]) dt + \frac{\text{Re}[\tilde{V}_2 e^{j\omega t}]}{Z_L} = 0 \\
 & = \text{Re}[\frac{1}{Z_2} \int (\tilde{V}_2 - \tilde{V}_1) dt + \frac{\tilde{V}_2}{Z_L}] e^{j\omega t} = 0 \\
 & = \text{Re}[-\tilde{I}_2 + \frac{\tilde{V}_2}{Z_L}] e^{j\omega t} = 0 \\
 & = -\tilde{I}_2 + \frac{\tilde{V}_2}{Z_L} = 0 \rightarrow \tilde{I}_2 = \frac{\tilde{V}_2}{Z_L}
 \end{aligned}$$

11.1.2. $Z_1 = C \parallel (L+Z)$ where $L = j\omega L$, $C = \frac{1}{j\omega C}$
and $Z = Z_L$

$$Z_0 = L + Z_1 = L + C \parallel (L+Z) = L + \frac{C(L+Z)}{C+L+Z} = \frac{2LC + L^2 + LZ + CZ}{C+L+Z}$$

11.1.3. $\tilde{I}_1 = \frac{\tilde{V}_0}{Z_0} = \frac{V_0(C+L+Z)}{L(2C+L+Z)+CZ}$

$$\tilde{V}_1 = \tilde{V}_0 - L\tilde{I}_1 = V_0 - \frac{V_0 \cdot L[C+L+Z]}{L[2C+L+Z]+CZ} = \frac{V_0[CL+CZ]}{L[2C+L+Z]+CZ}$$

$$\begin{aligned} \tilde{I}_2 = \tilde{I}_1 - \frac{1}{C}\tilde{V}_1 &= \frac{V_0[C+L+Z]}{L[2C+L+Z]+CZ} - \frac{V_0C[L+Z]}{C[L(2C+L+Z)+CZ]} \\ &= \frac{V_0C}{L(2C+L+Z)+CZ} \end{aligned}$$

$$\tilde{V}_2 = \tilde{V}_1 - L\tilde{I}_2 = \frac{V_0[CL+CZ]}{L[2C+L+Z]+CZ} - \frac{V_0CL}{L(2C+L+Z)+CZ} = \frac{V_0CZ}{L(2C+L+Z)+CZ}$$

check: $\tilde{I}_2 = \frac{\tilde{V}_2}{Z} = \frac{V_0CZ}{Z[L(2C+L+Z)+CZ]} = \frac{V_0C}{L(2C+L+Z)+CZ}$

$$\tilde{V}_1(t) = \tilde{V}_1 e^{j\omega t} = \frac{V_0[CL+CZ]}{L[2C+L+Z]+CZ} e^{j\omega t}$$

$1/Z_C$

check: $\tilde{I}_2 = \tilde{I}_1 - C \frac{d}{dt} \tilde{V}_1(t) = \frac{V_0(C+L+Z)}{L(2C+L+Z)+CZ} - j\omega C \left[\frac{V_0[CL+CZ]}{L[2C+L+Z]+CZ} \right]$

$$\tilde{I}_2 = \frac{V_0(C+L+Z)}{L(2C+L+Z)+CZ} - \frac{V_0C[L+Z]}{C[L(2C+L+Z)+CZ]} = \frac{V_0C}{L(2C+L+Z)+CZ}$$

$$\tilde{I}_1(t) = \tilde{I}_1 e^{j\omega t} = \frac{V_0(C+L+Z)}{L(2C+L+Z)+CZ} e^{j\omega t}$$


Z_{inductor}

check: $\tilde{V}_1 = \tilde{V}_0 - L \frac{d}{dt} \tilde{I}_1(t) = V_0 - j\omega L \left[\frac{V_0(C+L+Z)}{L(2C+L+Z)+CZ} \right] = \frac{V_0[CL+CZ]}{L(2C+L+Z)+CZ}$

$$\tilde{I}_2(t) = \tilde{I}_2 e^{j\omega t} = \frac{V_0 C e^{j\omega t}}{L(2C+L+Z)+CZ}$$

$$\tilde{V}_2(t) = \tilde{V}_2 e^{j\omega t} = \frac{V_0 CZ e^{j\omega t}}{L(2C+L+Z)+CZ}$$
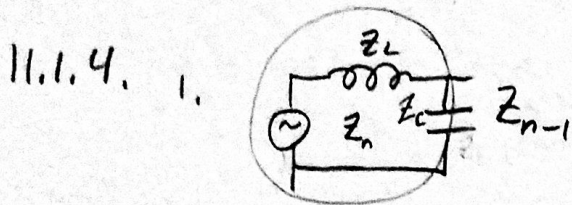
$$\begin{aligned} \text{check: } \tilde{V}_2 &= \tilde{V}_1 - L \frac{d}{dt} \tilde{I}_2(t) = \frac{V_0 [CL+CZ]}{L[2C+L+Z]+CZ} - \overset{L}{j\omega L} \left[\frac{V_0 C}{L(2C+L+Z)+CZ} \right] \\ &= \frac{V_0 CZ}{L(2C+L+Z)+CZ} \end{aligned}$$



$$Z_n = Z_L + Z_C \parallel Z_{n-1} = Z_L + \frac{Z_{n-1} \cdot Z_C}{Z_{n-1} + Z_C}$$

$$Z_n = j\omega L + \frac{(\frac{1}{j\omega C} \cdot Z_{n-1})}{Z_{n-1} + (\frac{1}{j\omega C})} = j\omega L + \frac{Z_{n-1}}{Z_{n-1}(j\omega C)+1}$$

$$2. \tilde{V}_2 = \tilde{V}_1 - j\omega L \tilde{I}_2$$

$$\tilde{V}_2 = \tilde{V}_1 - j\omega L [\tilde{I}_1 - j\omega C \tilde{V}_1]$$

$$\tilde{V}_2 = \tilde{V}_1 [1 - \omega^2 CL] - j\omega L \tilde{I}_1$$

$$\tilde{V}_{n+1} = \tilde{V}_n [1 - \omega^2 CL] - j\omega C \tilde{I}_n$$

$$3. \tilde{I}_2 = \tilde{I}_1 - j\omega C \tilde{V}_1$$

$$\tilde{I}_2 = \tilde{I}_1 - j\omega C [\tilde{V}_2 + j\omega L \tilde{I}_2]$$

$$\tilde{I}_2 = \tilde{I}_1 - j\omega C \tilde{V}_2 + \omega^2 CL \tilde{I}_2$$

$$\tilde{I}_2 (1 - \omega^2 CL) = \tilde{I}_1 - j\omega C \tilde{V}_2$$

$$\tilde{I}_2 = \frac{\tilde{I}_1 - j\omega C \tilde{V}_2}{(1 - \omega^2 CL)} \rightarrow \tilde{I}_{n+1} = \frac{\tilde{I}_n - j\omega C \tilde{V}_{n+1}}{(1 - \omega^2 CL)}$$