

9.2.1.

$$\begin{aligned}\tilde{V}_n(z) &= \tilde{V}_n^+ e^{-j\beta_n z} + \tilde{V}_n^- e^{j\beta_n z} \\ &= \tilde{V}_n^+ e^{-j\beta_n z} \left(1 + \frac{\tilde{V}_n^-}{\tilde{V}_n^+} e^{2j\beta_n z}\right) = \tilde{V}_n^+ e^{-j\beta_n z} (1 + \tilde{\Gamma}(z))\end{aligned}$$

$$\begin{aligned}\tilde{I}_n(z) &= \frac{1}{Z_n} (\tilde{V}_n^+ e^{-j\beta_n z} - \tilde{V}_n^- e^{j\beta_n z}) \\ &= \frac{\tilde{V}_n^+}{Z_n} e^{-j\beta_n z} \left(1 - \frac{\tilde{V}_n^-}{\tilde{V}_n^+} e^{2j\beta_n z}\right) = \frac{\tilde{V}_n^+}{Z_n} e^{-j\beta_n z} (1 - \tilde{\Gamma}(z))\end{aligned}$$

where $\tilde{\Gamma}(z) = \frac{\tilde{V}_n^-}{\tilde{V}_n^+} e^{2j\beta_n z}$

Impedance $Z_n(z) = \frac{\tilde{V}_n(z)}{\tilde{I}_n(z)} = Z_n \left[\frac{1 + \tilde{\Gamma}_n(z)}{1 - \tilde{\Gamma}_n(z)} \right]$

At the boundary:

$$\tilde{V}_0(z_{01}) = \tilde{V}_1(z_{01}) \quad \text{and} \quad \tilde{I}_0(z_{01}) = \tilde{I}_1(z_{01})$$

$$\tilde{V}_0(z_{01}) = \tilde{V}_0^+ e^{-j\beta_0 z_{01}} (1 + \tilde{\Gamma}_0(z_{01}))$$

$$\tilde{V}_1(z_{01}) = \tilde{V}_1^+ e^{-j\beta_1 z_{01}} (1 + \tilde{\Gamma}_1(z_{01}))$$

$$\tilde{I}_0(z_{01}) = \frac{\tilde{V}_0^+}{Z_0} e^{-j\beta_0 z_{01}} (1 - \tilde{\Gamma}_0(z_{01}))$$

$$\tilde{I}_1(z_{01}) = \frac{\tilde{V}_1^+}{Z_1} e^{-j\beta_1 z_{01}} (1 - \tilde{\Gamma}_1(z_{01}))$$

$$\tilde{Z}_0(z_{01}) = \frac{\tilde{V}_0(z_{01})}{\tilde{I}_0(z_{01})} = \frac{\tilde{V}_0^+ e^{-j\beta_0 z_{01}} (1 + \tilde{\Gamma}_0(z_{01}))}{\left(\frac{\tilde{V}_0^+}{Z_0}\right) e^{-j\beta_0 z_{01}} (1 - \tilde{\Gamma}_0(z_{01}))} = Z_0 \left[\frac{1 + \tilde{\Gamma}_0(z_{01})}{1 - \tilde{\Gamma}_0(z_{01})} \right]$$

Since $\tilde{V}_0(z_{01}) = \tilde{V}_1(z_{01})$ and $\tilde{I}_0(z_{01}) = \tilde{I}_1(z_{01})$

$$\tilde{Z}_0(z_{01}) = \tilde{Z}_1(z_{01})$$

$$Z_0 \left[\frac{1 + \tilde{\Gamma}_0(z_0)}{1 - \tilde{\Gamma}_0(z_0)} \right] = Z_1$$

$$\tilde{\Gamma}_0(z_0) = \frac{Z_1(z_0) - Z_0}{Z_1(z_0) + Z_0}$$

$$\tilde{\Gamma}_0(z) = \frac{\tilde{V}_0^-}{\tilde{V}_0^+} e^{2j\beta_0 z} \rightarrow \tilde{V}_0^-(z) = \tilde{V}_0^+ e^{2j\beta_0 z_0} \left[1 + \frac{Z_1(z_0) - Z_0}{Z_1(z_0) + Z_0} \right] \text{ since } \tilde{V}_0^+ \text{ is known}$$

$$\tilde{\Gamma}_1(z) = \frac{\tilde{V}_1^-}{\tilde{V}_1^+} e^{2j\beta_1 z} \rightarrow \tilde{V}_1^-(z) = \tilde{V}_1^+ e^{2j\beta_1 z_2} \left[1 + \frac{Z_2(z_2) - Z_1}{Z_2(z_2) + Z_1} \right]$$

$$\tilde{V}_2^-(z) = \tilde{V}_2^+ e^{2j\beta_2 z_3} \left[1 + \frac{Z_3(z_3) + Z_2}{Z_3(z_3) - Z_2} \right]$$

$$\frac{\tilde{V}_0^-(z)}{\tilde{V}_0^+(z)} e^{-j\beta_0 z_0} = \tilde{\Gamma}_0(z_0) \rightarrow \frac{\tilde{V}_0^-(z)}{\tilde{V}_0^+(z)} = e^{j\beta_0 z_0} \left[\frac{Z_1(z_0) - Z_0}{Z_1(z_0) + Z_0} \right]$$

$$\frac{\tilde{V}_1^-(z)}{\tilde{V}_1^+(z)} e^{-j\beta_1 z_2} = \tilde{\Gamma}_1(z_2) \rightarrow \frac{\tilde{V}_1^-(z)}{\tilde{V}_1^+(z)} = e^{j\beta_1 z_2} \left[\frac{Z_2(z_2) - Z_1}{Z_2(z_2) + Z_1} \right]$$

9.2.2. 1. $V(z, t) = V^+ [\cos(\omega t - \beta z) + \rho \cos(\omega t + \beta z)]$

$$\cos(\alpha \pm \beta) = \cos \alpha \cos \beta \mp \sin \alpha \sin \beta$$

$$V(z, t) = V^+ [\cos(\omega t) \cos(\beta z) + \sin(\omega t) \sin(\beta z) + \rho \cos(\omega t) \cos(\beta z) - \rho \sin(\omega t) \sin(\beta z)]$$

$$V(z, t) = V^+ [(1 + \rho) \cos(\omega t) \cos(\beta z) + (1 - \rho) \sin(\omega t) \sin(\beta z)]$$

$$V(z, t) = A \cos(\omega t) \cos(\beta z) + B \sin(\omega t) \sin(\beta z) \text{ where } A = V^+(1 + \rho) \text{ and } B = V^+(1 - \rho)$$

3. This plot shows 2 oppositely travelling waves which will produce a standing wave. The VSWR can be calculated from the wave amplitudes to determine the impedance mismatch and describe how efficiently radio-frequency power is transmitted.